

Lab 6
Jared Rocha
Luis Gomez

Exp 11: A Simple Data Latching and Display Circuit

Summary: We implemented the sseg_dec.v module provided and created an a dflop with a button. So when the button was pressed the switch input would be latched into memory The input could only change if the button was pressed again to release the input being held by the latch.

Figure below is the BDD for exp 11

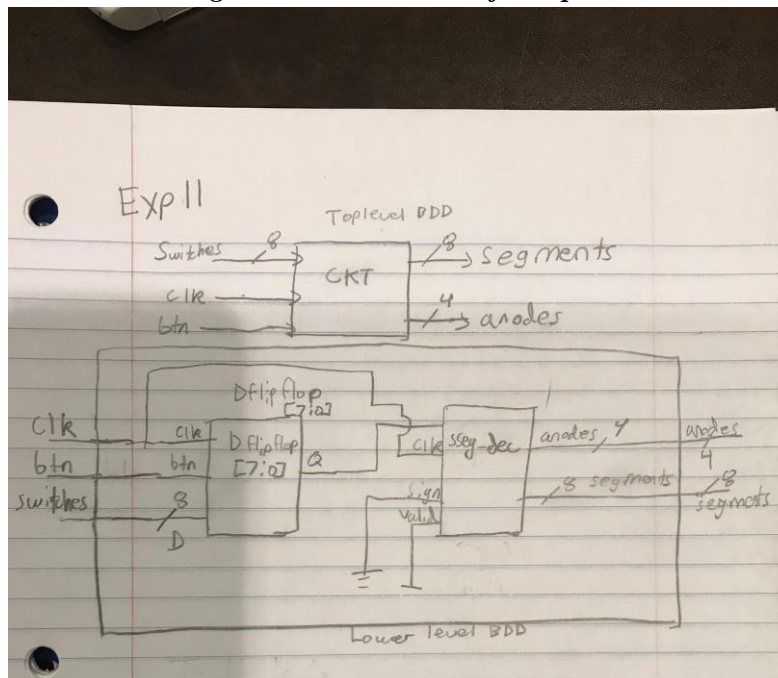



Figure below, Excitation Table for exp 11

Q	Qnext	D
0	0	0
0	1	1
1	0	0
1	1	1

Verification: Our verification process entailed extensive physical board tests as demonstrated in the video link below.

Video: <https://youtu.be/nwjEh1qY0zE>

Figure below is the Circuit Diagram of exp 11 provided by Vivado

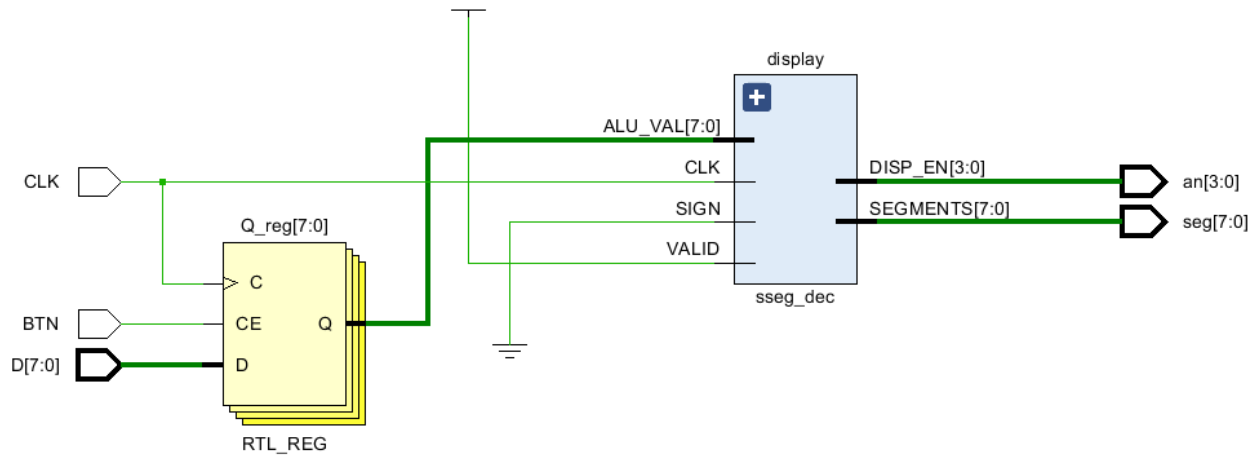

Code

```

22  /*
23  module sseg_dec( input [7:0] ALU_VAL,
24                  input SIGN,
25                  input VALID,
26                  input CLK,
27                  output [3:0] DISP_EN,
28                  output [7:0] SEGMENTS);
29  */
30
31  module exp11(
32      input CLOCK,
33      input [7:0] SWA,
34      input btnC, // Q
35      output [3:0] an,
36      output [7:0] seg
37  );
38
39      reg [7:0] dFlopInput;
40
41      sseg_dec display( dFlopInput, 0, 1, CLOCK, an, seg );
42
43      always @ (posedge CLOCK)
44      begin
45          if(btnC == 1'b1) // if button is pressed, SWA is latched to Flip Flop
46              dFlopInput = SWA;
47      end
48
49  endmodule
50

```

Questions:

1. When you press the button, how many times is the data effectively “latched” in the associated D flip-flops? HINT: realize that the clock input from the development board operates at 100Mhz

100000000 times if button is pushed for 1 second. $f(t) = t(100000000/\text{seconds})$.

Video: <https://youtu.be/x8SDC0OMgwc>

Code

```

21 //
22 module sseg_dec( input [7:0] ALU_VAL,
23                 input SIGN,
24                 input VALID,
25                 input CLK,
26                 output [3:0] DISP_EN,
27                 output [7:0] SEGMENTS);
28
29
30 module TFlop_4BCounter(
31     input CLOCK,
32     input btnEn, btnT, // En & T inputs (left & right)
33     output [3:0] an,
34     output [7:0] seg
35 );
36
37     reg [3:0] counter;
38     reg [19:0] refreshTimer;
39     wire bit;
40
41     reg [4:0] TFlopInput;
42     reg Q = 1'b0;
43     reg Qnext;
44
45     sseg_dec display( TFlopInput, 0, 1, CLOCK, an, seg );
46
47     assign bit = refreshTimer[19:18];
48
49     always @ (posedge CLOCK)
50     begin
51
52         Qnext <= btnT & btnEn; // inverted button states
53         Q <= Qnext;
54
55         if( Qnext == 1'b1 ) begin
56             TFlopInput <= counter;
57             refreshTimer <= refreshTimer + 1;
58             if (bit == 1'b1)
59                 counter <= counter + bit;
60         end
61         else TFlopInput <= ~counter;
62     end
63 endmodule

```

Questions:

1. How many flip-flops did this FSM design use?


Although we were unsuccessful in implementing the required design we believe that the total number of FF's in the FSM would be at least $12 + n$, where n is the bit-size of your timer variable in the counter module. Specifically, the FF's arose from the following: T-flop module, 4-FF's, Counter-Module includes a variable number depending on the bit-size of your refresh-Timer variable, and the sseg module included 8-FF's.

2. Without thinking about it, this counter simply “rolled over” when the highest count was reached. What was it that made it magically roll over? Briefly explain

By counting to 15 it rolls back because there are only 4 bits. So when the value is $15 = 1111$, adding a single bit results in a carryout and the value becomes 0000.

 3. Describe the changes that would be required to implement this counter using JK flip-flops instead of T flip-flops.

Add an AND gate that inputs are Q and K. Add an AND gate that inputs are $\sim Q$ and J. OR the two AND gates outputs. Make the output of OR gate the input for toggle button.



4. This counter is referred to as an “up counter” (counts from low binary number to high binary numbers). Describe the changes that would be required in order to make it a “down counter”.

We suppose a down-counter could be created by inverting the T-flop result so that pressing T results in the default value not the inverted result. Then what you would see on the BCD output from the sseg module is the inverted result decreasing in value as the default value increases.